



**Department of Physics and Astronomy, National Institute of Technology Rourkela**  
**End-semester Examination, Autumn 2023-2024**  
**PH5006: Analog and Digital Electronics**


**Total marks: 50**

**Time: 3 hours**


**Note: Answer all questions**

---

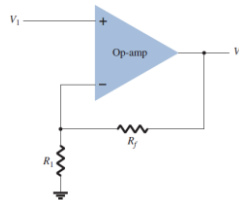1. (A) Derive an expression for the voltage gain of the non-inverting amplifier. [3]  
(B) Explain the virtual ground of an operational amplifier. [2]  
(C) For the following circuit, calculate the input voltage,  $V_1$  for  $V_0 = 12\text{ V}$ ,  $R_1 = 100\text{ k}\Omega$ ,  $R_f = 500\text{ k}\Omega$ . [2]




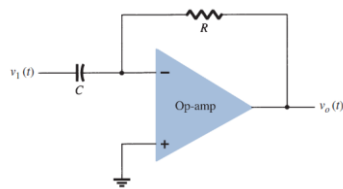- (D) For the following differentiator circuit, calculate  $v_o(t)$  for  $v_1(t) = 5\sin(\omega t)$ ,  $R = 500\text{ k}\Omega$  and  $C = 10\mu\text{F}$ . [2]



- (E) Draw a circuit diagram for a voltage buffer amplifier. [1]
2. (A) Show the connection of three op-amp stages using an LM348 IC to provide outputs that are 10, 20, and 50 times larger than the input, use a feedback resistor of  $R_f = 500\text{ k}\Omega$  in all stages. [3]  
(B) Define the cut-off frequency of an active filter. Draw the circuit diagram and derive an expression for the cut-off frequency of low pass and high pass filter. [1+4]

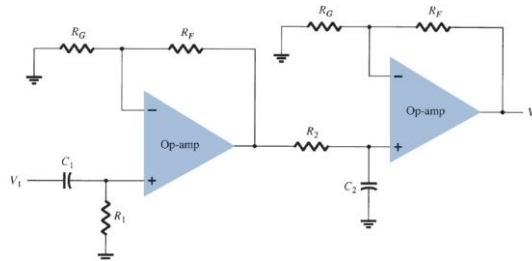(C) Calculate the cutoff frequencies of the band pass filter circuit as shown below with  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 15\text{ k}\Omega$ ,  $C_1 = 0.1\text{ }\mu\text{F}$ , and  $C_2 = 0.002\text{ }\mu\text{F}$ . [2]



3. (A) Discuss the differences between the ordinary amplifier and the power amplifier. [2]  
 (B) Derive an expression for the efficiency of the transformer coupled class A power amplifier. How does it differ from the direct coupled class A amplifier and the push-pull class B amplifier. [4+2]  
 (C) A transformer coupled class A amplifier supplies 3-Watt power to the speaker. If the supply voltage is 30 V and  $I_{CQ}$  is 200 mA, then find the efficiency of this amplifier. [2]
  
4. (A) How does the closed loop gain depend on the temperature of negative feedback amplifier. [2]  
 (B) For a negative feedback amplifier, if the gain of the amplifier is 500 and transfer function of feedback network is 0.6, then calculate the amount of feedback. [2]  
 (C) For negative feedback amplifier, the following parameters are given: open loop gain = 100, minimum and maximum frequency are 80 Hz and 60kHz respectively. If 2% of the output is returned to the input in opposition, then find the modified value of gain and the cut-off frequency. [2]  
 (D) Derive an expression of the closed loop gain of a series-shunt feedback amplifier. [2]  
 (E) What are the Barkhausen criteria for the oscillator? Draw the circuit diagram of a RC phase shift oscillator using BJT. [2]
  
5. (A) Convert the followings to the Octal and decimal number system  
      $(14.3)_{10}$  and  $(13AB.D)_{16}$  [2+2]  
 (B) What is a truth table for NOR gates? Show a switching circuit using NOR gate. [2]  
 (C) Design the Ex-OR and Ex-NOR gates using NAND gate. [2]  
 (D) What are the differences between half adder and full adder? [2]